
 




HDL, RTL and FPGA: Lab 2

Review of your next steps
in designing digital hardware

Marker: 670 ns | Cursor: 290500 ps

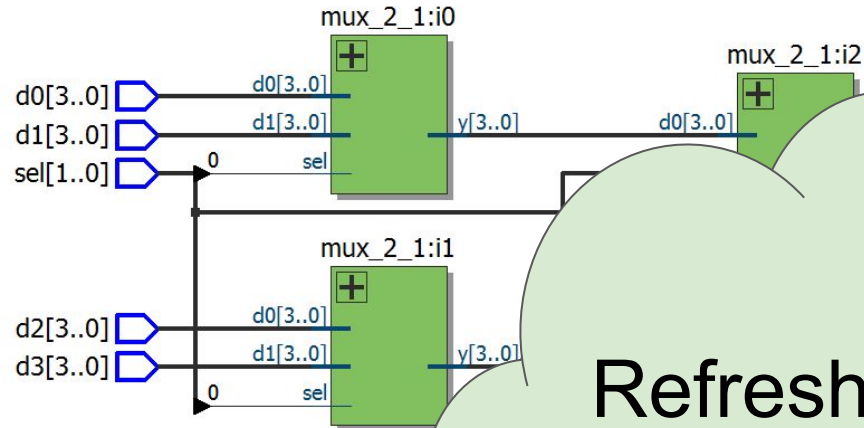

Refreshing knowledge from Lab 1

 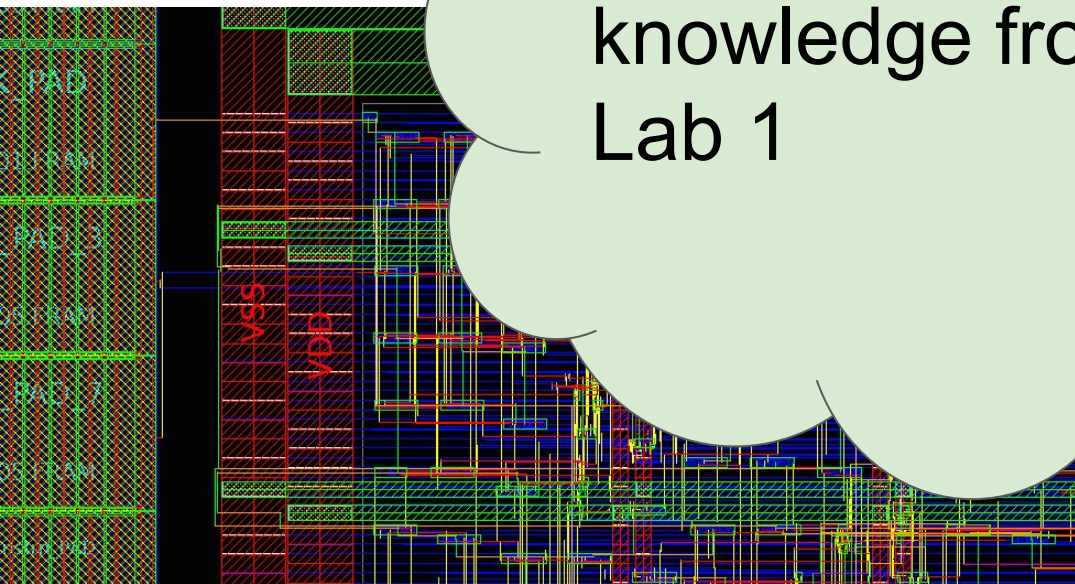


Hardware/software dualism - an informal example

Microcontroller (embedded chip, ASIC, SoC)

CPU

Designed in Verilog

Executes instructions

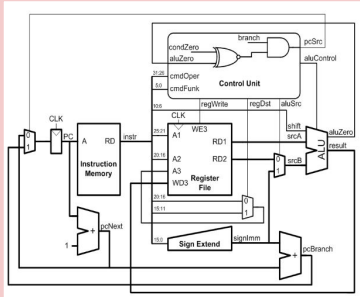


Memory

Contains a program,
a sequence of instructions

Compiled from C
or a similar language

```
18800005  
00001025  
00451021  
0044182a  
5460fffe  
00451021  
03e00008  
00000000
```

 Hardware/software dualism - an informal example / 2





Software: from C to processor instructions

C:	Assembly:	Machine code
<pre>int f (int a, int b) { int s = 0; while (s < a) s += b; return s; }</pre>	<pre>sum: blez \$4, exit move \$2, \$0 addu \$2, \$2, \$5 loop: slt \$3, \$2, \$4 bnel \$3, \$0, loop addu \$2, \$2, \$5 exit: jr \$31 nop</pre>	<pre>18800005 00001025 00451021 0044182a 5460fffe 00451021 03e00008 00000000</pre>

Circuits: from Verilog to transistors (simplified)
  
```
module counter
(
  input clock,
  input reset,
  output logic [1:0] n
);
always @(posedge clock)
begin
  if (reset)
    n <= 0;
  else
    n <= n + 1;
end
endmodule
```




What is an FPGA? A simplified explanation

A matrix of cells with changeable function

One cell can become AND, another OR, yet another - one bit of memory

An FPGA does not contain a fixed CPU, but can be configured to work as a CPU

 A picture from <http://jjmk.dk/MMMI/PLDs/FPGA/fpga.htm>





IOB
Input Output Block

CLB
Configurable
Logic Block


PSM
Programable
Switch Matrix

Connection lines
Single, Long
Double, Direct

Marker: 670 ns | Cursor: 290500 ps

  


From combination
to sequential logic

 

From Lab 1: Combinational logic

 - The outputs of the group of components depend only on inputs
- You set inputs and get outputs after some time
- This group is called “a combinational cloud”
- Used to calculate logic and arithmetical functions




```
module top
(
    input  a, b, c, d,
    output e, f
);

    assign e = a & (b | c);
    assign f = ~ (c ^ d);

endmodule
```

Computation in combinational logic is not instant


 
- Before the results are ready, the outputs may contain random values.
- How to find when the results are ready and can be used by the next step of computation?
- We can synchronize the computation with a special signal called clock.



The picture is from Digital Design and Computer Architecture, 2nd Edition by David Harris and Sarah Harris. Elsevier, 2012


Clock is a periodic signal with square waveform

 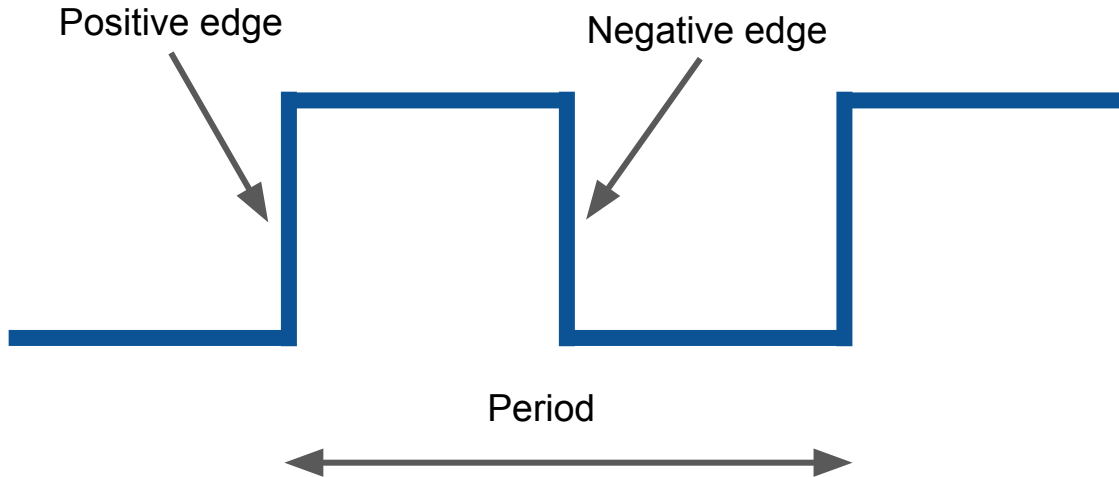- This period is long enough for any combinational computation to complete.
- Clock frequency = $1 / \text{period}$.
- Clock is usually generated by a crystal oscillator (find it on the board).




A circuit synchronized with a clock is called sequential

 - The sequential circuit go through a sequence of states.
- The current state is stored in D-flip-flops.
- A new state is computed based on the previous state and the circuit's inputs.
- A new state is recorded into D-flip-flops when clock goes from low to high.
- The outputs are computed based on the inputs and the current state




Huffman model of sequential circuits

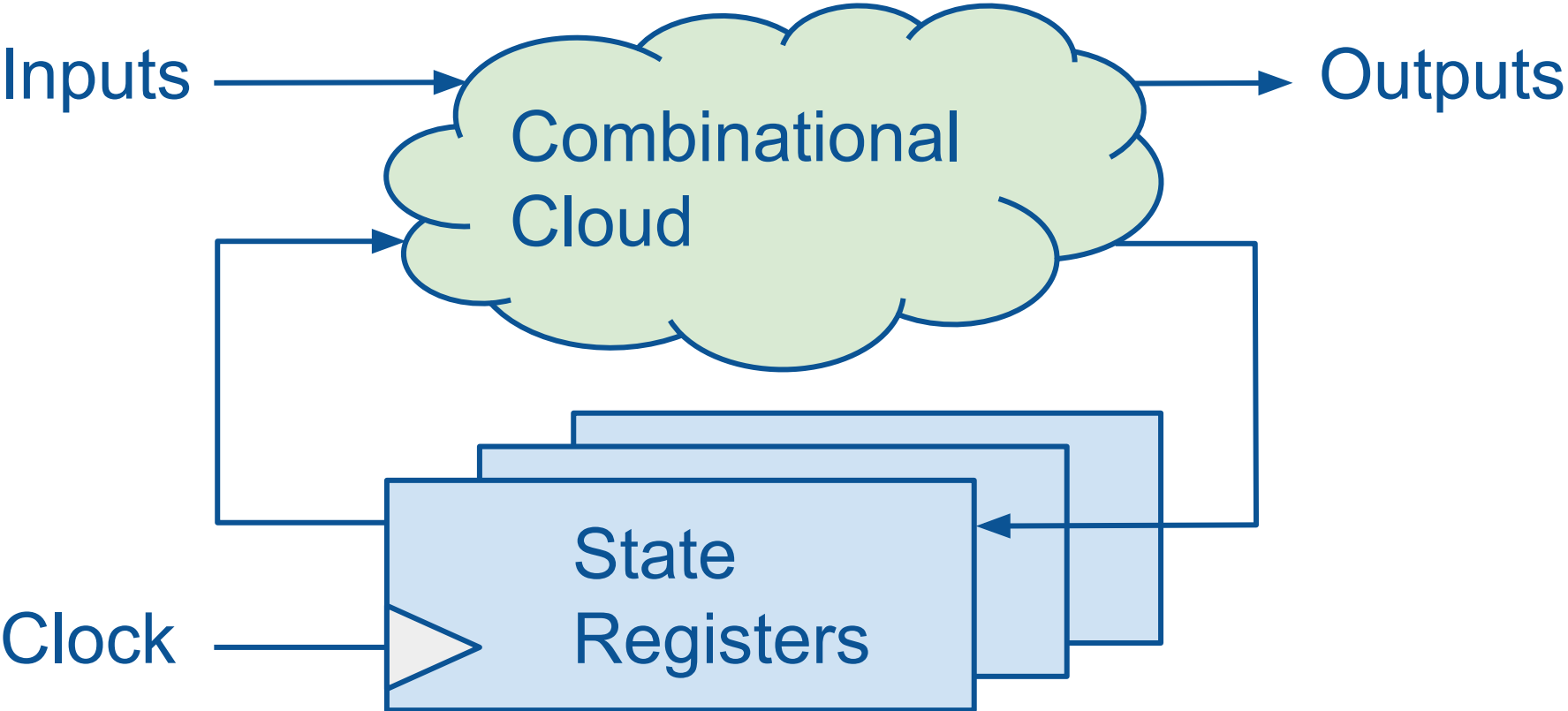



What the sequential logic allows us to do

 - Counting
- Memorizing the information
- Adding new data and repeating the computation
- Waiting for an event coming from outside the device
- In short: sequential logic is what makes computer to do interesting things





A picture of John Searle's Chinese room thought experiment is from <http://deskarati.com/2014/07/01/john-searles-chinese-room-thought-experiment>

Marker: 670 ns | Cursor: 290500 ps

  

The Exercises

 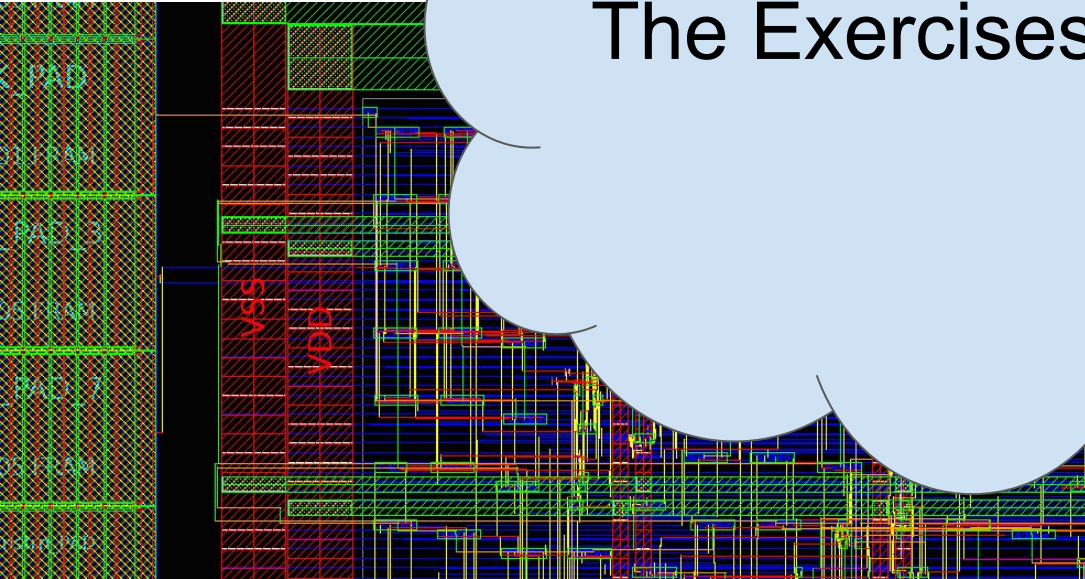

Lab 2 exercises

1. The function of D-flip-flop, the basic brick of sequential design
2. Counter, a combination of combinational and sequential
3. Connecting flip-flops back-to-back to make a shift register
4. Finite State Machine (FSM) for sequence recognition
5. The application of FSM for interfacing sensors
6. The concept of pipelining
7. Looking forward schoolMIPS and MIPSfpga

D-flip-flop records the data at the end of clock cycle

- “Always at positive edge of `clk` store the value of signal `d` in a D-flip-flop inferred by variable `q`. `q` is also connected to the output”.
- `always` block is similar to the `initial` block, however it is evaluated on every event described after `@`.
- The assignment `<=` is called non-blocking, it will take effect after all current `always` blocks get evaluated

```
module d_flip_flop
(
    input    clk,
    input    d,
    output   reg q
);

always @ (posedge clk)
    q <= d;
```

Reset signal guarantees the initial state

- This design uses reset active low (“negedge rst_n”), some others use reset active high.
- Reset is necessary for control signals, so the device does not act erratically on power-up.

```
module dff_async_rst_n
(
    input        clk,
    input        rst_n,
    input        d,
    output reg   q
);


always @ (posedge clk or negedge rst_n)
    if (!rst_n)
        q <= 0;
    else
        q <= d;
```


A group of D-flip-flops is called a register.




- Do not confuse with Verilog `reg` or CPU registers in programming.
- We can parameterize the number of D-flip-flops in a register using Verilog `parameter` declaration.

```
module dff_async_rst_n_param
#(
    parameter WIDTH = 8,
           RESET = 8'b0
)
(
    input                clk,
    input                rst_n,
    input [WIDTH - 1 : 0] d,
    output reg [WIDTH - 1 : 0] q
);
```

 Register keeps the value during the cycle



Compare

   

Generating and using clock in a testbench

You can also use clock to schedule assigning stimuli, the values for the DUT ports (DUT = Design under Test).

```
initial
begin
    clk = 0;

    forever
        # 10 clk = ! clk;
end
```

```
initial
begin
    clk_en  <= 1'b1;
    arg_vld <= 1'b0;


    repeat (2) @ (posedge clk);
    rst_n <= 0;
    repeat (2) @ (posedge clk);
    rst_n <= 1;
end
```


Adder + Register = Counter


- A group of D-flip-flops is called a register.
- Do not confuse with Verilog `reg` or CPU registers in programming.
- In this code the result of addition is stored to use in the next clock cycle.


```
module counter
(
    input          clock,
    input          reset_n,
    output reg [31:0] count
);

 always @(posedge clock or negedge reset_n)
begin
    if (!reset_n)
        count <= 32'b0;
    else
        count <= count + 32'b1;
end
```




 Register contains 0, it gets propagated to the adder.




 

 
0 enters the adder. The adder's output is not stable yet.



 
The adder computed $0 + 1 = 1$. Register still contains 0.



 
Positive edge of the clock is coming. Register is still 0.



 
The aperture time. Register is about to store 1.



 
Register recorded 1 and is about to propagate it outside.



 
The current state is 1, it gets propagated to the adder.



 
1 enters the adder. The adder's output is not stable yet.



 
The adder computed $1 + 1 = 2$. Register still contains 1.



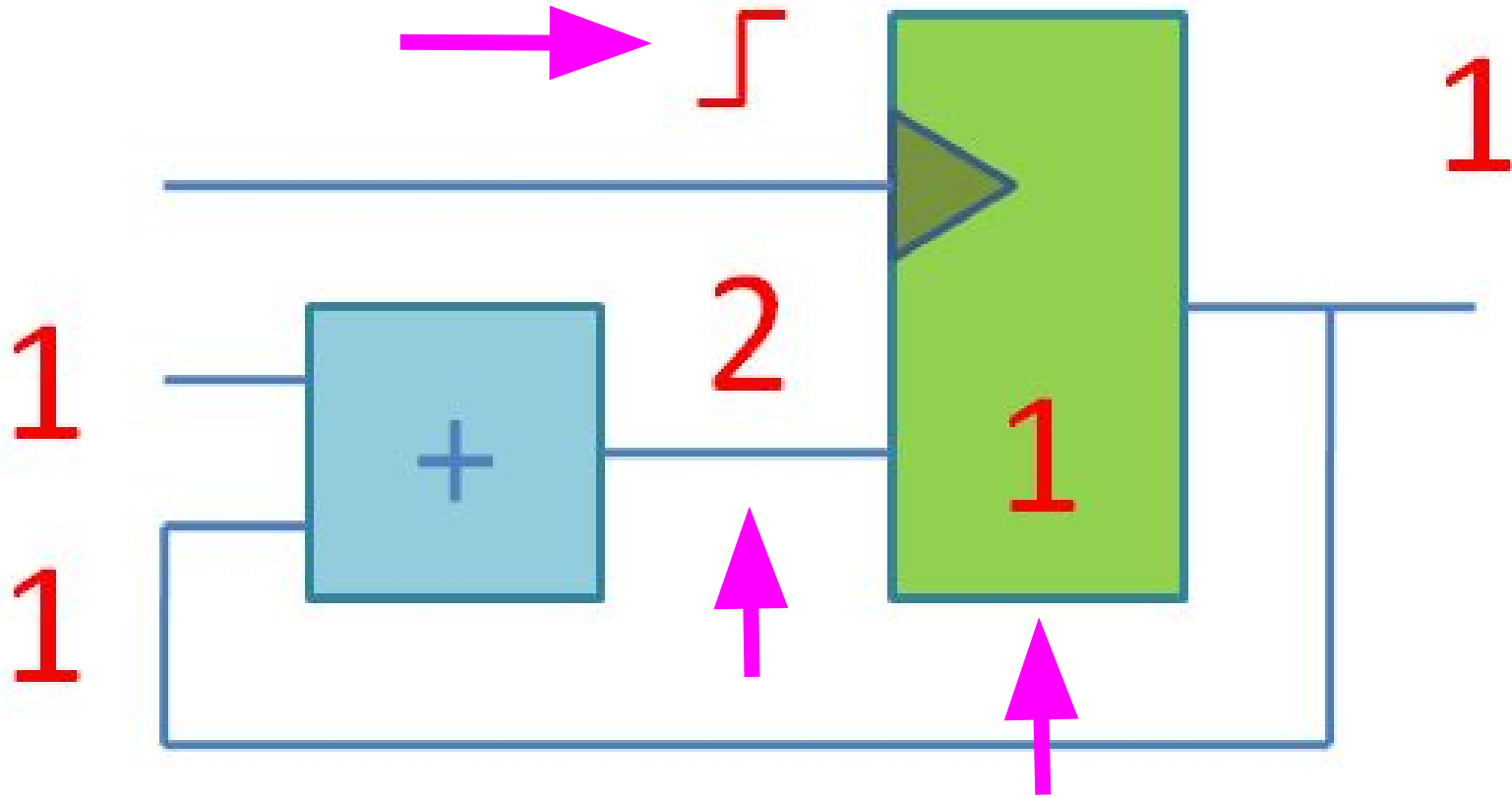
Positive edge of the clock is coming. Register is still 1.



 
The aperture time. Register is about to store 2.



 Register recorded 2 and is about to propagate it outside.




 The current state is 2, it gets propagated to the adder.




Finite State Machine, the decision maker

- Let's implement an example of FSM that recognizes sequences.
- We got this example from Digital Design and Computer Architecture by David Harris and Sarah Harris, 2012.
- “A snail crawls down a paper tape with 1's and 0's on it. The snail smiles whenever the last two digits it has crawled over are 01. Design a state machine of the snail's brain.”
- FSMs are special cases of Huffman sequential circuits.
- Mealy FSM uses inputs directly to compute outputs, Moore's FSM does not.

 


FSM designers use state transition diagrams

Moore FSM

 

Mealy FSM

 

- Circles designate states.
- Arcs designate transitions depending on inputs.
- For Mealy FSM arcs indicate inputs / outputs.

Coding FSMs in Verilog - State register

```
module pattern_fsm_moore
(
    input  clock,
    input  reset_n,
    input  enable,
    input  a,
    output y
);
    parameter [1:0] S0 = 0, S1 = 1, S2 = 2;
    reg [1:0] state, next_state;

    // State register
    always @ (posedge clock or negedge reset_n)
        if (! reset_n)
            state <= S0;
        else if (enable)
            state <= next_state;
```

Coding FSMs in Verilog - Next state logic

```
// Next state logic

always @*
  case (state)

S0:
  if (a)
    next_state = S0;
  else
    next_state = S1;

S1:
  if (a)
    next_state = S2;
  else
    next_state = S1;

S2:
  if (a)
    next_state = S0;
  else
    next_state = S1;

  default:
    next_state = S0;



  endcase

// Output logic based on current state


assign y = (state == S2);
```

  Examples: interfaces to sensors


- Ultrasonic distance sensor
 - https://github.com/yuri-panchul/2017-year-end/blob/master/terasic_de10_lite/hc_sr04_receiver.v
- Digilent Ambient Light Sensor with SPI protocol
 - https://github.com/yuri-panchul/2017-tomsk-novosibirsk-astana/blob/master/parts_and_examples/pmod_als_spi_receiver/pmod_als_spi_receiver.v



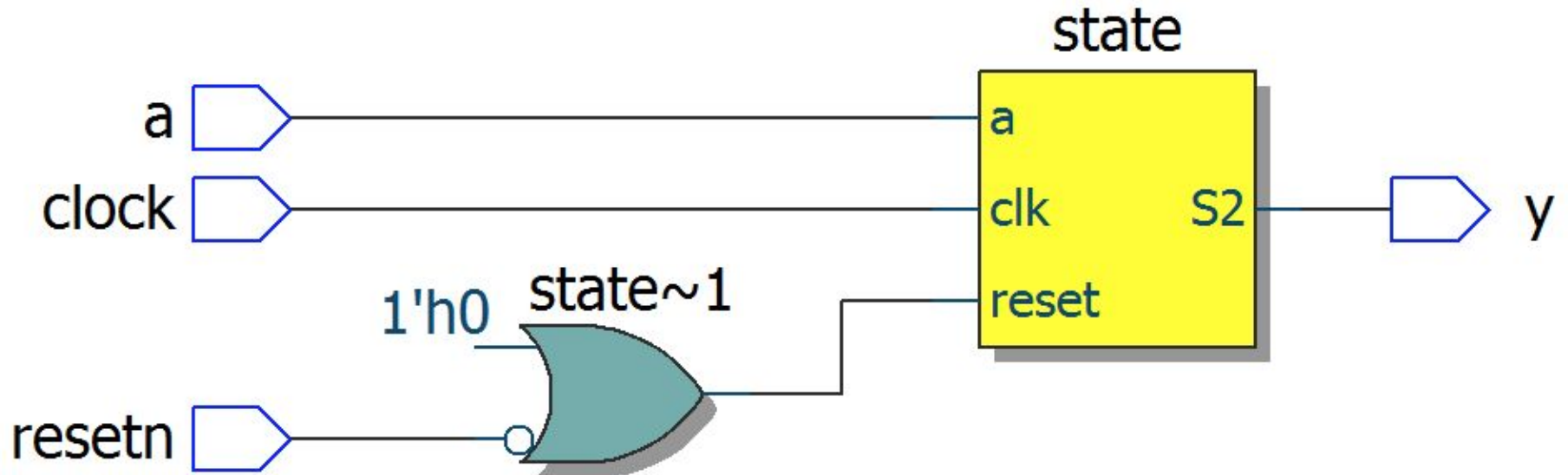
Synthesis tools recognize FSMs and optimize them




The concept of pipelining - 1

 

The concept of pipelining - 2

 


The concept of pipelining - 3

 


CPU pipeline, best-known example of the pipelining principle

 The execution unit of MIPS M5150 CPU core processes the stream of instructions



Learn about CPUs using schoolMIPS and MIPSfpga

 - schoolMIPS is as simple RISC CPU as you can get, use it to learn the basics.
- MIPSfpga is to experiment with an industrial core, it uses a variant of MIPS M5150 from the previous slide



Thank
You!

